



**DIGITAL DESIGN**

**ASSIGNMENTREPORT**

**ASSIGNMENT ID : 3**

**Student Name: 徐驰 (Xu Chi)**

**Student ID: 11912224**

## PART 1: DIGITAL DESIGN THEORY

Provide your answers here:

1.  $F(A, B, C, D) = \sum (1, 3, 5, 8, 9, 10, 11, 13, 15)$

K-map

AB \ CD	00	01	11	10
00	0	1	1	0
01	0	1	0	0
11	0	1	1	0
10	1	1	1	1

AND-OR:  $F = AB' + C'D + AD + B'D$

OR-AND:  $F = (A + D)(B' + D)(A + B' + C')$

NOR-OR:  $F = (A' + B)' + (C + D')' + (A' + D')' + (B + D')'$

NOR-NOR:  $F = ((A + D)' + (B' + D)' + (A + B' + C'))'$

NAND-NAND:  $F = ((AB')' (C'D)' (AD)' (B'D'))'$


NAND-AND:  $F = (A'D')' (BD')' (A'BC)'$

2.

parity generator					parity checker				
input				output1	input				output
A	B	C	D	P	A	B	C	P	R

0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0	1	1
0	0	1	0	1	0	0	1	1	0
0	0	1	1	0	0	0	1	0	1
0	1	0	0	1	0	1	0	1	0
0	1	0	1	0	0	1	0	0	1
0	1	1	0	0	0	1	1	0	0
0	1	1	1	1	0	1	1	1	1
1	0	0	0	1	1	0	0	1	0
1	0	0	1	0	1	0	0	0	1
1	0	1	0	0	1	0	1	0	0
1	0	1	1	1	1	0	1	1	1
1	1	0	0	0	1	1	0	0	0
1	1	0	1	1	1	1	0	1	1
1	1	1	0	1	1	1	1	1	0
1	1	1	1	0	1	1	1	0	1
 
$$F = (A \oplus B \oplus C \oplus D) \oplus A \oplus B \oplus C = D$$



3.

input			output		
x	y	z	A	B	C
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	1	0	1
1	1	1	1	1	0

$$F = \{A, B, C\}$$

A:x\yz	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$A = xy + xz + yz$$


B:x\yz	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$B = x \oplus y \oplus z$$


C:x\yz	00	01	11	10
0	1	0	0	1

1	1	0	0	1
---	---	---	---	---

$C = z'$

 

4. Here is the principle:

 

$$C = A_3A_2A_1A_0 \times B_3B_2B_1B_0$$


$$= \{C_7, C_6, C_5, C_4, C_3, C_2, C_1, C_0\}$$

$$C_0 = A_0B_0, C_1 = A_1B_0 + A_0B_1, C_2 = A_2B_0 + A_1B_1 + A_0B_2, C_3 = A_3B_0 + A_2B_1 + A_1B_2 + A_0B_3,$$

$$C4 = A3B1 + A2B2 + A1B3, C5 = A3B2 + A2B3, C6 = A3B3$$

NB:  $C_i$  is not concluded carry bit!

Here is the circuit diagram:

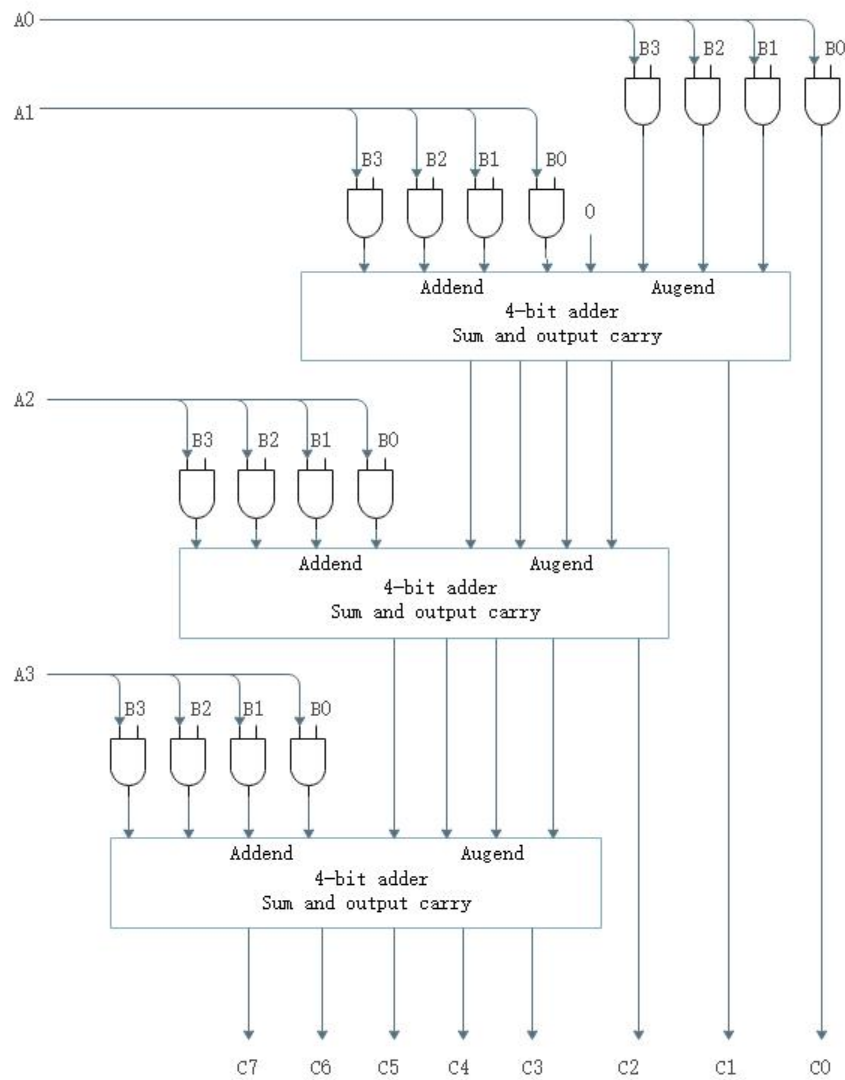

5.

```
module mux
```

```
(EN,S3,S2,S1,S0,D15,D14,D13,D12,D11,D10,D9,D8,D7,D6,D5,D4,D3,D2,D1,D0,Y,W);
```

```
input EN,S3,S2,S1,S0,D15,D14,D13,D12,D11,D10,D9,D8,D7,D6,D5,D4,D3,D2,D1,D0;
```

```
output reg Y;
```

```
output W;
```

```
always @*
```

```
if (~EN)
```

```
    case({S3,S2,S1,S0})
```

```
        4'b0000: Y = D0;
```

```
        4'b0001: Y = D1;
```

```
        4'b0010: Y = D2;
```

```
        4'b0011: Y = D3;
```

```
        4'b0100: Y = D4;
```

```
        4'b0101: Y = D5;
```

```
        4'b0110: Y = D6;
```

```
        4'b0111: Y = D7;
```

```
        4'b1000: Y = D8;
```

```
        4'b1001: Y = D9;
```

```
        4'b1010: Y = D10;
```

```
        4'b1011: Y = D11;
```

```
        4'b1100: Y = D12;
```

```
        4'b1101: Y = D13;
```

```

4'b1110: Y = D14;

4'b1111: Y = D15;

endcase

else

Y = 1'b0;

assign W = ~Y;

endmodule

```

(a)  $F(A, B, C, D) = \sum (1, 2, 5, 8, 10, 14)$

$= 0 * A'B'C'D' + 1 * A'B'C'D + 1 * A'B'CD' + 0 * A'B'CD + 0 * A'BC'D' + 1 * A'BC'D + 0 * A'BCD' + 0 * A'BCD$   
 $+ 1 * AB'C'D' + 0 * AB'C'D + 1 * AB'CD' + 0 * AB'CD + 0 * ABC'D' + 0 * ABC'D + 1 * ABCD' + 0 * ABCD$

$= D0 * m0 + D1 * m1 + D2 * m2 + D3 * m3 + D4 * m4 + D5 * m5 + D6 * m6 + D7 * m7 + D8 * m8 + D9 * m9$   
 $+ D10 * m10 + D11 * m11 + D12 * m12 + D13 * m13 + D14 * m14 + D15 * m15$

$= m0 * 0 + m1 * 1 + m2 * 1 + m3 * 0 + m4 * 0 + m5 * 1 + m6 * 0 + m7 * 0 + m8 * 1 + m9 * 0 + m10 * 1 + m11 * 0$   
 $+ m12 * 0 + m13 * 0 + m14 * 1 + m15 * 0$

```

module fun_abcd_mux(input A,B,C,D,output F);

wire sen,sd15,sd14,sd13,sd12,sd11,sd10,sd9,sd8,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0;

wire snf;

assign {sen,sd15,sd14,sd13,sd12,sd11,sd10,sd9,sd8,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0} =
17'b0_0100_0101_0010_0110;

```



```

mux xc(.EN(sen),

.S3(A),.S2(B),.S1(C),.S0(D),

.D15(sd15),.D14(sd14),.D13(sd13),.D12(sd12),

.D11(sd11),.D10(sd10),.D9(sd9),.D8(sd8),

.D7(sd7),.D6(sd6),.D5(sd5),.D4(sd4),

.D3(sd3),.D2(sd2),.D1(sd1),.D0(sd0),

.Y(F),.W(snf));

endmodule

```

$$(b) F(A, B, C, D) = \prod (4, 5, 11) = \sum (0, 1, 2, 3, 6, 7, 8, 9, 10, 12, 13, 14, 15)$$

$$\begin{aligned}
&= 1 * A'B'C'D' + 1 * A'B'C'D + 1 * A'B'CD' + 1 * A'B'CD + 0 * A'BC'D' + 0 * A'BC'D + 1 * A'BCD' + 1 * \\
&A'BCD + 1 * AB'C'D' + 1 * AB'C'D + 1 * AB'CD' + 0 * AB'CD + 1 * ABC'D' + 1 * ABC'D + 1 * ABCD' + 1 * \\
&ABCD
\end{aligned}$$

$$\begin{aligned}
&= D0 * m0 + D1 * m1 + D2 * m2 + D3 * m3 + D4 * m4 + D5 * m5 + D6 * m6 + D7 * m7 + D8 * m8 + D9 * \\
&m9 + D10 * m10 + D11 * m11 + D12 * m12 + D13 * m13 + D14 * m14 + D15 * m15
\end{aligned}$$

$$\begin{aligned}
&= m0 * 1 + m1 * 1 + m2 * 1 + m3 * 1 + m4 * 0 + m5 * 0 + m6 * 1 + m7 * 1 + m8 * 1 + m9 * 1 + m10 * 1 + \\
&m11 * 0 + m12 * 1 + m13 * 1 + m14 * 1 + m15 * 1
\end{aligned}$$

```

module fun_abcd_mux(input A,B,C,D,output F);

wire sen,sd15,sd14,sd13,sd12,sd11,sd10,sd9,sd8,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0;

wire snf;

assign {sen,sd15,sd14,sd13,sd12,sd11,sd10,sd9,sd8,sd7,sd6,sd5,sd4,sd3,sd2,sd1,sd0} =

```

```
17'b0_1111_0111_1100_1111;
```

```
mux xc(.EN(sen),
```

```
.S3(A),.S2(B),.S1(C),.S0(D),
```

```
.D15(sd15),.D14(sd14),.D13(sd13),.D12(sd12),
```

```
.D11(sd11),.D10(sd10),.D9(sd9),.D8(sd8),
```

```
.D7(sd7),.D6(sd6),.D5(sd5),.D4(sd4),
```

```
.D3(sd3),.D2(sd2),.D1(sd1),.D0(sd0),
```

```
.Y(F),.W(snf));
```

```
endmodule
```

6. Since there are two outputs(Dif and Bo), we have to select 2 multiplexers. Start with the truth table of full subtractor. Use karnaugh maps. Select 2 variables as your select line. For example x and y in my case.

The truth table:

input			output	
x	y	z	Dif	Bo
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0

1	1	0	0	0
1	1	1	1	1


With K-map:

Dif:x\yz	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\text{Dif} = x \oplus y \oplus z$$

Bo:x\yz	00	01	11	10
0	0	1	1	1
1	0	0	1	0



$$\text{Bo} = x'z + x'y + yz$$

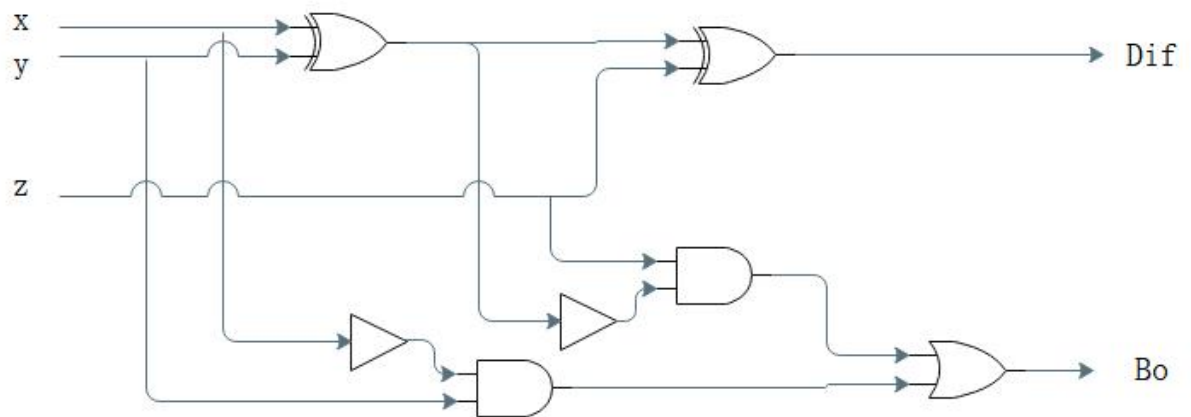

Implement by two  $4 \times 1$  multiplexers

input			output	
x	y	z	Dif	Bo
0	0	0	0=z	0=z

0	0	1	$1=z$	$1=z$
0	1	0	$1=z'$	$1=1$
0	1	1	$0=z'$	$1=1$
1	0	0	$1=z'$	$0=0$
1	0	1	$0=z'$	$0=0$
1	1	0	$0=z$	$0=z$
1	1	1	$1=z$	$1=z$

  

## PART 2: DIGITAL DESIGN LAB (TASK1) (CHECKED)

### DESIGN

---

*Describe the design of your system by providing the following information:*

- *Verilog design (provide the Verilog code)*
- *Truth-table*

### SIMULATION

---

*Describe how you build the test bench and do the simulation.*

- *Using Verilog(provide the Verilog code)*
- *Wave form of simulation result (provide screen shots)*
- *The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation.*

### CONSTRAINT FILE AND THE TESTING

---

*Describe how you test your design on the Minisys Practice platform.*

- *Constraint file (provide the screen shots on the feature of a pin and the binding info between pins and the input /output ports)*
- *The testing result (provide the screen shots (at least 3 testing scene) to show state of inputs and outputs along with the related descriptions.*

### THE DESCRIPTION OF OPERATION

---

*Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.*

- *Problems and solutions*

## PART 2: DIGITAL DESIGN LAB (TASK2) (CHECKED)

### DESIGN

---

*Describe the design of your system by providing the following information:*

- *Verilog design while using data flow (provide the Verilog code)*
- *Verilog design while using structured design (provide the Verilog code)*
- *Block design (provide screen shots)*
- *Truth-table*

### SIMULATION

---

*Describe how you build the test bench and do the simulation.*

- *Using Verilog (provide the Verilog code)*
- *Wave form of simulation result (provide screen shots)*
- *The description on whether the simulation result is same as the truth-table, is the function of the design meet the expectation*

### CONSTRAINT FILE AND THE TESTING

---

*Describe how you test your design on the Minisys Practice platform.*

- *Constraint file (provide the screen shots on the feature of a pin and the binding info between pins and the input /output ports)*
- *The testing result (provide the screen shots (at least 3 testing scene)) to show state of inputs and outputs along with the related descriptions.*

### THE DESCRIPTION OF OPERATION

---

*Describe the problem occurred while in the lab and your solution. Any suggestions are welcomed.*

- *Problems and solutions*